

5/5/2022

EXPERIMENT NO.1

EC111

VISHAL KUMAR PRAJAPATI

ROLL NO. 2101227

GROUP NO. 18

Name - Vishal Kumar Prajapati

Roll - 2101227


Aim:

To draw static forward characteristic of diode.

Apparatus:

1N4007, 1K Ω resistor, power supply, breadboard

Circuit Diagram:

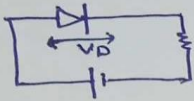

V_{in}	V_D (V)	I_D (mA)
0	-0.3783	0
0.2	0.3458	4.89 μ A
0.4	0.4524	78.78 μ A
0.8	0.4924	206.45 μ A
0.8	0.5230	0.387
1.0	0.5410	0.739
1.2	0.5564	0.786
1.4	0.5684	0.9060
1.6	0.5790	1.0941
1.8	0.5864	1.2785
2.0	0.5975	1.4156
4	0.6344	3.525
6	0.6576	5.495
8	0.6721	7.612
10	0.6832	9.535
12	0.6920	11.553

Verified
05/05/2022

EXPERIMENT NO. 1

TITLE: TO STUDY V-I CHARACTERISTICS OF A DIODE

OBJECTIVE:


To design the circuit and verify the V-I characteristics.

APPARATUS REQUIRED:

- Resister 1kohm
- power supply
- breadboard
- diode IN4007
- wires, etc.



THEORY:

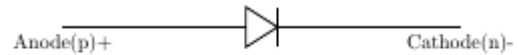The diode is a device formed from a junction of n-type and p-type semiconductor material. The lead connected to the p-type material is called the anode and the lead connected to the n-type material is the cathode. In general, the cathode of a diode is marked by a solid line on the diode.




FUNCTION OF P-N JUNCTION DIODE IN FORWARD BIAS:

The positive terminal of the battery is connected to the P side(anode) and the negative terminal of the battery is connected to the N side(cathode) of a diode, the holes in the p-type region and the electrons in the n-type region are pushed toward the junction and start to neutralize the depletion zone, reducing its width. The positive potential applied to the p-type material repels the holes, while the negative potential applied to the n-type material repels the electrons. The change in potential between the p side and the n side decreases or switches signs. With increasing forward-bias voltage, the depletion zone eventually becomes thin enough that the zone's electric field cannot counteract charge carrier motion across the p–n junction, which as a consequence reduces electrical resistance. The electrons that cross the p–n junction into the p-type material (or holes that cross into the n-type material) will diffuse into the nearby neutral region. The amount of minority diffusion in the near-neutral zones determines the amount of current that may flow through the diode. □

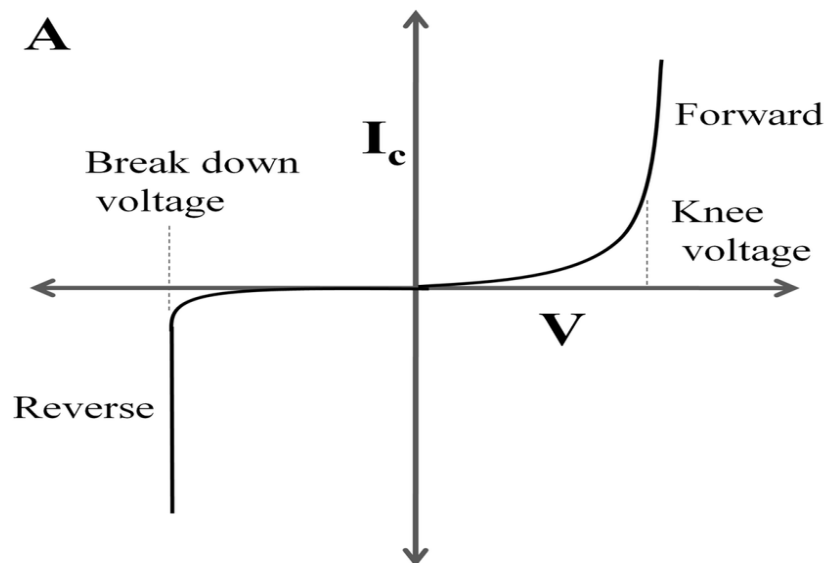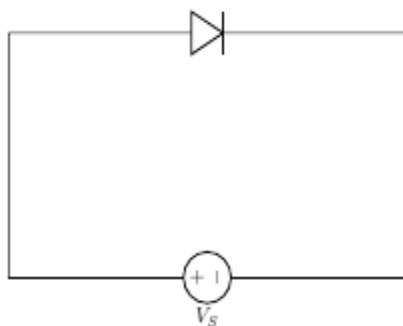

CIRCUIT DIAGRAM:

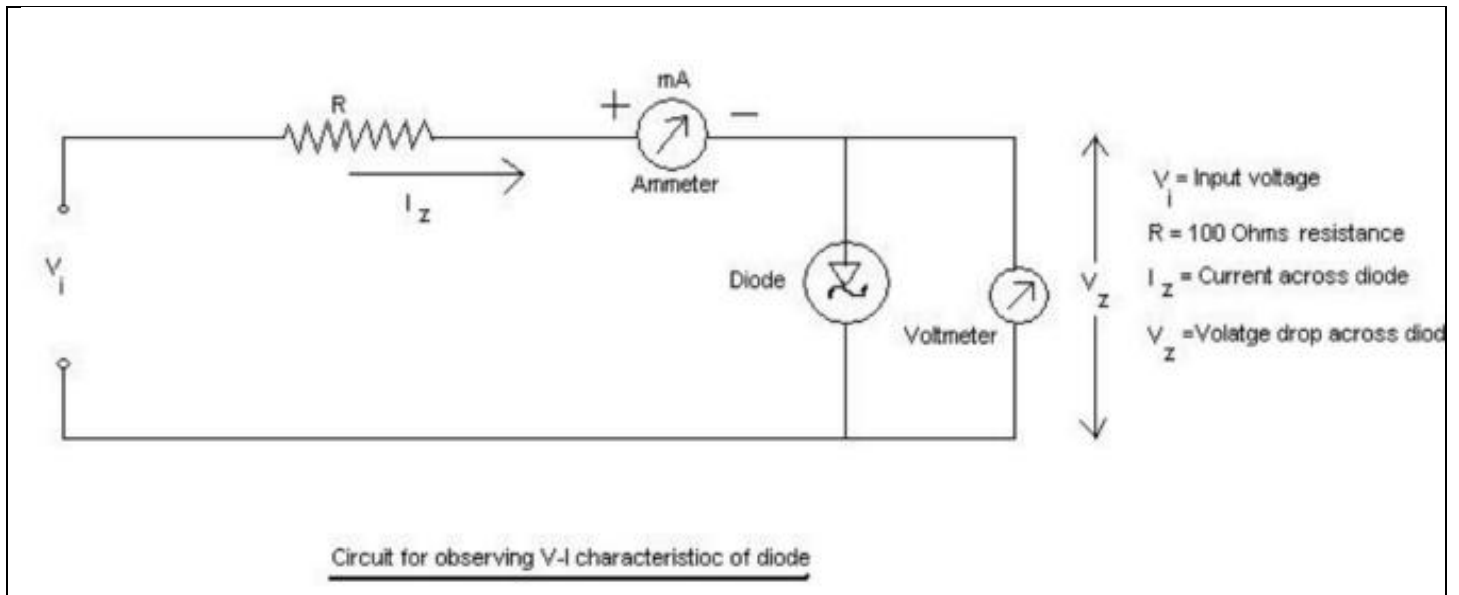

OBSERVATION:

S.NO.	VOLTAGE V_{IN} (V)	VOLTAGE ACROSS DIODE V_D (V)	CURRENT ACROSS DIODE I_D (mA)
1	0	-0.3783	0
2	0.2	0.3458	0.00489
3	0.4	0.4524	0.07878
4	0.6	0.4924	0.20645
5	0.8	0.5230	0.387

6	1.0	0.5410	0.739
7	1.2	0.5564	0.786
8	1.4	0.5684	0.906
9	1.6	0.5790	1.0941
10	1.8	0.5864	1.2785
11	2.0	0.5975	1.4156
12	4	0.6344	3.525
13	6	0.6576	5.495
14	8	0.6721	7.612
15	10	0.6832	9.535
16	12	0.6920	11.553

CALCULATIONS:

- STATIC FORWARD RESISTANCE $R_{DC} = V_D / I_D$
- DYNAMIC FORWARD RESISTANCE $R_{AC} = \Delta V_D / \Delta I_D$
- AVERAGE RESISTANCE $R_{AVG} = \Delta V_D / \Delta I_D$

S.NO.	VOLTAGE V_{IN} (V)	STATIC RESISTANCE (ohm)	DYNAMIC RESISTANCE (ohm)
1	0	Infinite	148078
2	0.2	1270.14	1442.69
3	0.4	1185.58	313.308
4	0.6	1077.74	169.482
5	0.8	838.836	51.134
6	1.0	937.913	327.66
7	1.2	1042.17	100
8	1.4	1045.19	56.353
9	1.6	1049.17	40.1302
10	1.8	1037.7	80.9628
11	2.0	1035.74	17.4931
12	4	984.0	11.7766
13	6	986.242	6.8493
14	8	981.242	5.7723
15	10	983.726	4.3605
16	12	981.39	59.8979

AVERAGE FORWARD RESISTANCE = 942.25 Ohm

RESULT:

Analyze the V-I characteristics of a diode.

