

EXPERIMENT NUMBER 5

- **OBJECTIVE:**

To Design and Simulate BCD to Excess 3, Excess 3 to BCD code converters.

- **APPARTUS REQUIRED:**

- Power supply
- LED
- Resistance
- Switches

- **THEORY:**

- **BCD Codes:**

Numeric codes represent numeric information i.e. only numbers as a series of 0's and 1's.
Numeric codes used to represent decimal digits are called Binary Coded Decimal (BCD)

codes. A BCD code is one, in which the digits of a decimal number are encoded-one at a time into group of four binary digits. There are a large number of BCD codes in order to represent decimal digits 0, 1, 2,.....9, it is necessary to use a sequence of at least four binary digits. Such a sequence of binary digits which represents a decimal digit is called code word.

- EXCESS-3 CODE:

It is a non-weighted code. It is also a self-complementing BCD code used in decimal arithmetic units. . The Excess-3 code for the decimal number is performed in the same manner as BCD except that decimal number 3 is added to the each decimal unit before encoding it to binary.

- BCD to Excess-3:

To convert from binary code A to binary code B, the input lines must supply the bit combination of elements as specified by code A and the output lines must generate the corresponding bit combination of code B. A combinational circuit performs this transformation by means of logic gates. As we want to design 4-bit code, we must use four input variables and four output variables. Designate the four input binary variables by the symbols A,B,C,D, and the four output variables by w, x, y, and z. The truth table relating the input and output variables is as shown. A two-level logic diagram may be obtained directly from the Boolean expressions derived by the maps. The expressions obtained may be manipulated for the purpose of using common gates for two or more outputs. This manipulation illustrates flexibility obtained with multiple-output systems when implemented with three or more levels of gates.

$$z = D$$

$$y = CD + C'D' = CD(C+D)'$$

$$x = B'(C+D) + B(C+D)'$$

$$w = A + BC + BD = A + B(C+D)$$

Table: BCD to Excess-3 Converter

Decimal	BCD				Excess-3			
Digit	A	B	C	D	w	x	y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

- Excess-3 TO BCD :**

We know that, excess-3 code begins with the binary 0011(decimal 3) and it will continue up to binary 1100(decimal 12) where I get the output binary 1001(decimal 9) for input binary 1100(decimal 12). So I need 4 variables as inputs and 4 variables as outputs. With 4 variables I can represent 16 binary values from 0000 to 1111. Since I do not use 0, 1, 2, 13, 14, 15 as inputs, when I simplify the output function I use those terms as don't care conditions.

$$A = WX + WYZ$$

$$B = X'Y' + XYZ + Z'$$


$$C = YZ' + Y'Z$$

$$D = Z'$$


Table: Excess-3 to BCD Converter

Inputs				Outputs			
W	X	Y	Z	A	B	C	D
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1

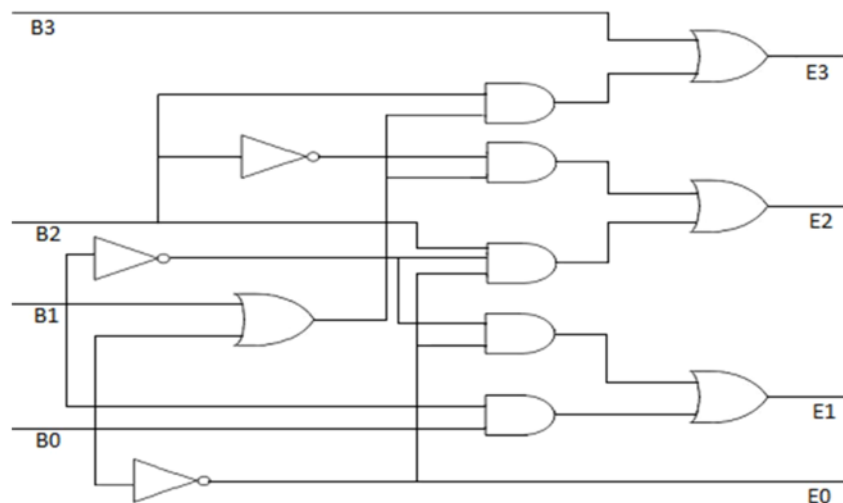- **CIRCUIT DIAGRAM:**
- **Logic Diagram for BCD to Excess-3 Code Converter:**



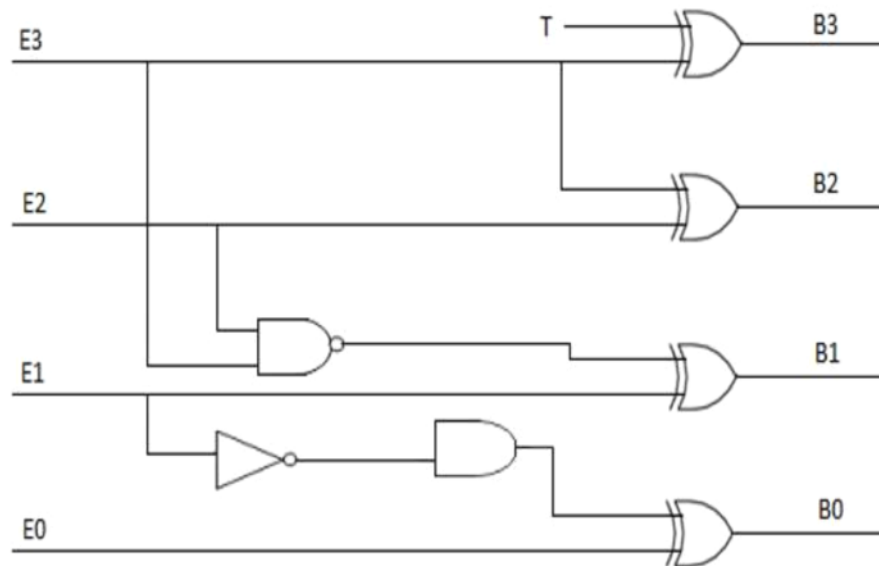
- Logic Diagram for Excess-3 Code to BCD Converter:



• CALCULATIONS:

- Verification for BCD to Excess-3 Code Converter:



An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD


Run
Clear

B3: 0 OFF

B2: 0 OFF

B1: 0 OFF

B0: 0 OFF

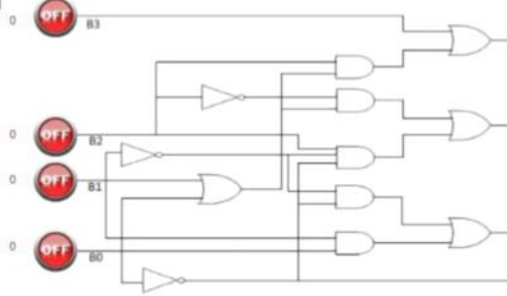

0000


Decimal : 0

BCD to Excess 3 Converter


0011

Decimal : 3

BCD Input

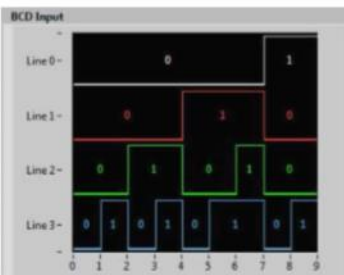

Excess 3 Input

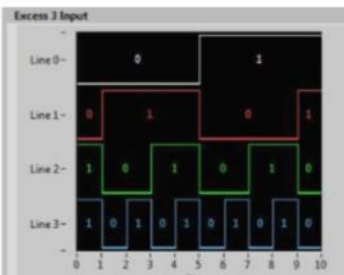


[About Us](#) | [Contact Us](#) | [Feedback](#)

Copyright © 2011 COEP Virtual Lab

<https://hrcn.vlabs.ac.in/Experiment2/index1.html>

1/1


2101227_VISHALKUMARPRAJAPATI_EXPNO5 Page 7


Virtual Labs
 An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess-3
Excess-3 to BCD

Run
Clear

BCD to Excess

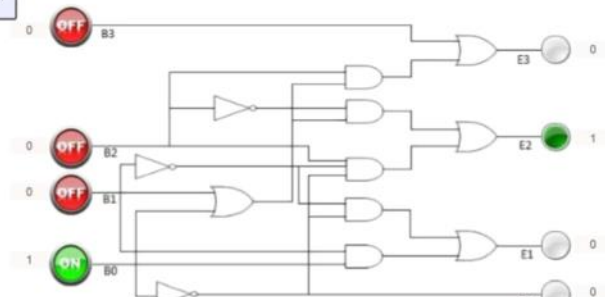


Truth Table							
BCD				Excess-3			
B3	B2	B1	B0	E3	E2	E1	E0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0


1000

Decimal : 1
BCD to Excess 3 Converter
0100
Decimal : 4

BCD Input

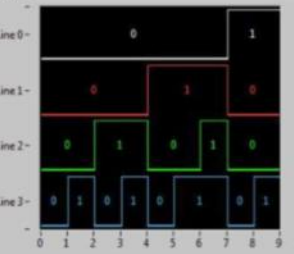


Excess 3 Input

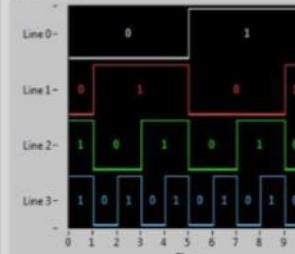

[About Us](#) / [Contact Us](#) / [Feedback](#)
 Copyright © 2011 COEP Virtual Lab

https://he-cvnlabs.ac.in/Experiment2/index1.html

1/1



An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

BCD to Excess

Run
Clear

B3

0 OFF

B2

0 OFF

B1

1 ON

B0

0 OFF

E3

0

E2

1

E1

0

E0

1

0100


Decimal : 2

BCD to Excess 3 Converter


0101

Decimal : 5

BCD Input

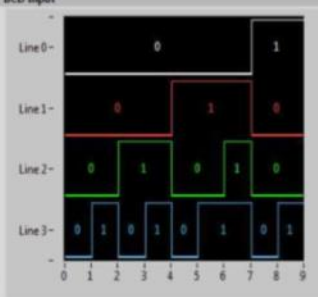


Excess 3 Input

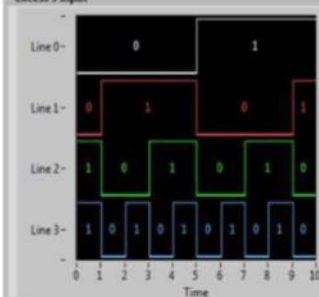

[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright ©2011 COEP Virtual Lab

<https://be-cen.vlabs.ac.in/Experiment2/index1.html>

1/1


Virtual Labs
 An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD


Run
Clear

0 OFF B3

0 OFF B2

1 ON B1

1 ON B0

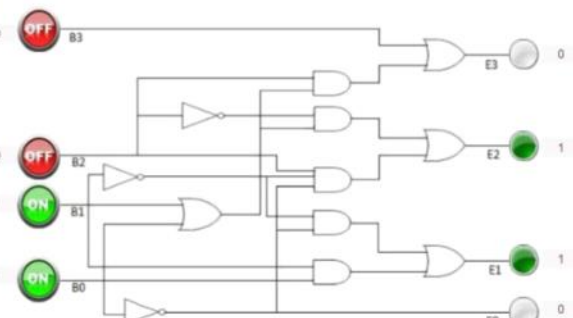

Truth Table							
BCD				Excess-3			
B3	B2	B1	B0	E3	E2	E1	E0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0


1100

BCD to Excess 3 Converter


0110

Decimal : 3
Decimal : 6

BCD Input

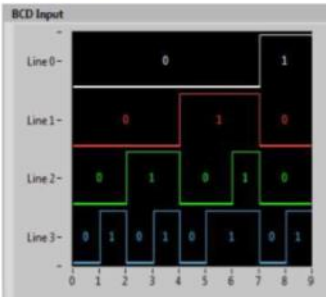

Excess 3 Input

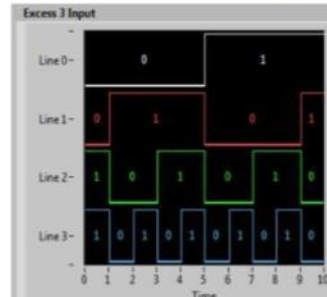


[About Us](#) / [Contact Us](#) / [Feedback](#)
 Copyright © 2011 COEP Virtual Lab

https://be-enr-vlabs.ac.in/Experiment2/index1.html

1/1


2101227_VISHALKUMARPAJAPATI_EXPNO5 Page 10


Virtual Labs
 An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

Run
Clear

BCD to Excess

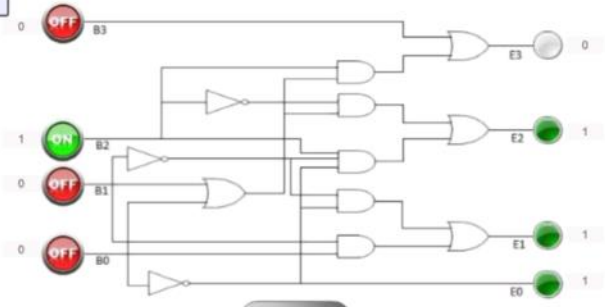

0010


Decimal : 4

BCD to Excess 3 Converter


0111

Decimal : 7

BCD Input

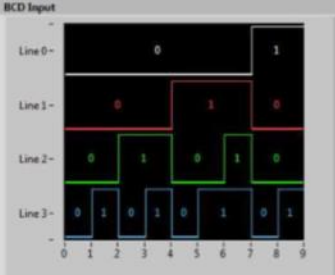


Excess 3 Input

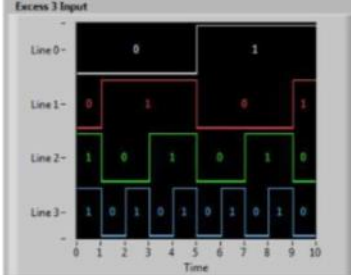

[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright ©2011 COEP Virtual Lab

<https://he-cnen-vlabs.ac.in/Experiment2/index1.html>

1/1




An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

BCD to Excess

Run
Clear

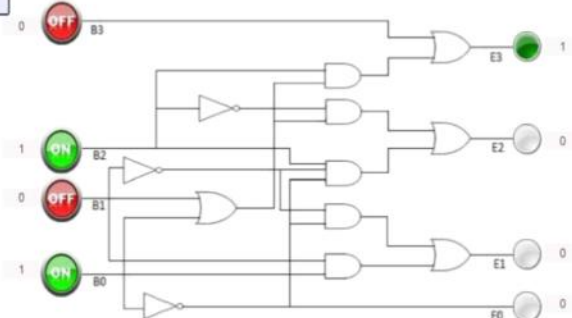

1010


Decimal : 5

BCD to Excess 3 Converter


1000

Decimal : 8


BCD Input

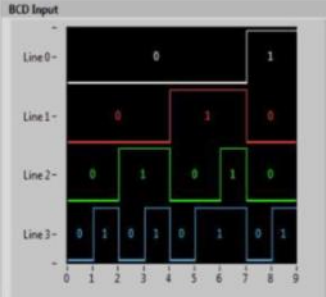

Excess 3 Input

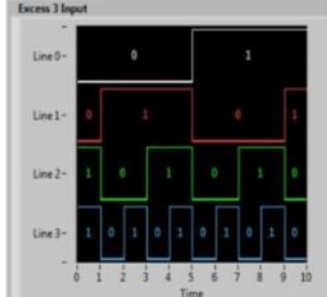

[About Us](#) |
 [Contact Us](#) |
 [Feedback](#)
 Copyright ©2011 COEP Virtual Lab


Virtual Labs
 An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD


BCD to Excess

0 OFF B3

1 ON B2

1 ON B1

0 OFF B0

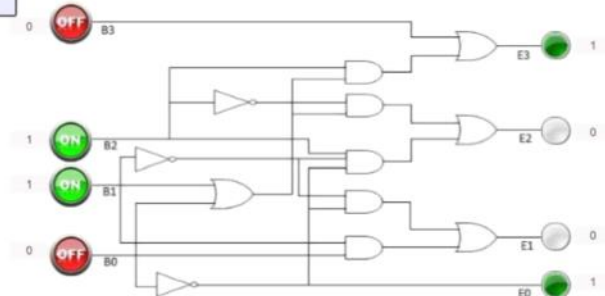

1 ON E3

0 OFF E2

0 OFF E1

1 ON E0

0110


Decimal : 6

BCD to Excess 3 Converter


Decimal : 9

1001

BCD Input

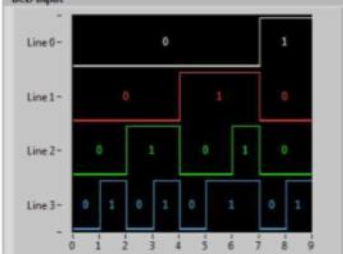

Excess 3 Input

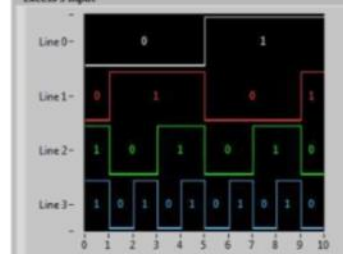


[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright © 2011 COEP Virtual Lab.

https://he-nen.vlabs.ac.in/Experiment7/index1.html

1/1

2101227_VISHALKUMARPRAJAPATI_EXPNO5 Page 13




Virtual Labs
An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

BCD to Excess

Run
Clear

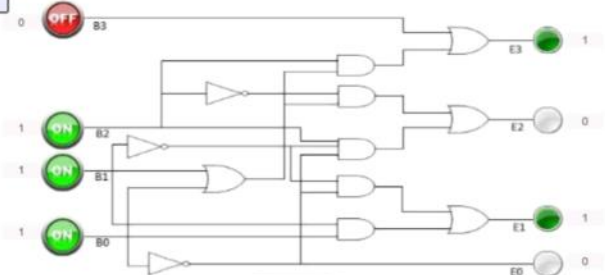

Truth Table

BCD				Excess-3			
B3	B2	B1	B0	E3	E2	E1	E0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0


1110

BCD to Excess 3 Converter


1010

Decimal : 7
Decimal : 10

BCD Input

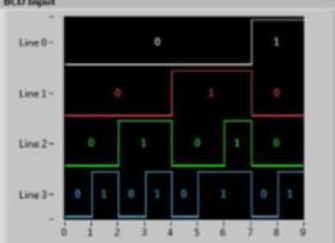

Excess 3 Input

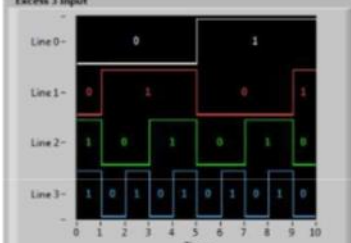


[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright © 2011 CRRP Virtual Lab

<https://he-nen-vlabs.in/experiment2/index1.html>

1/1

2101227_VISHALKUMARPRAJAPATI_EXPNO5 Page 14




Virtual Labs
An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

BCD to Excess

Run
Clear

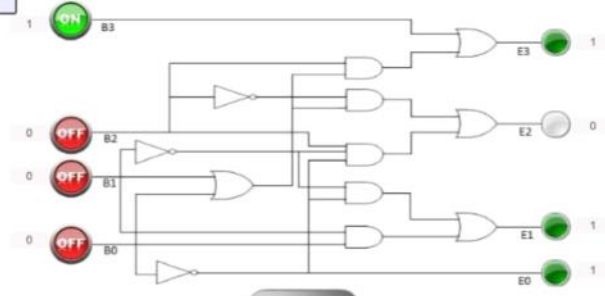

Truth Table							
BCD				Excess-3			
B3	B2	B1	B0	E3	E2	E1	E0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0


0001

BCD to Excess 3 Converter


1011

Decimal : 8
Decimal : 11

BCD Input

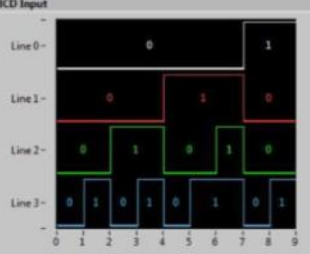

Excess 3 Input

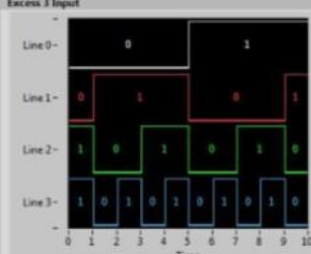


[About Us](#) / [Contact Us](#) / [Feedback](#)
 Copyright ©2011 COEP Virtual Lab

<https://he-coep-vlabs.ac.in/Experiment2/index1.html>

1/1

2101227_VISHALKUMARPRAJAPATI_EXPNO5 Page 15



An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

Run


Clear

B3: 1 (ON)

B2: 0 (OFF)

B1: 0 (OFF)

B0: 1 (ON)

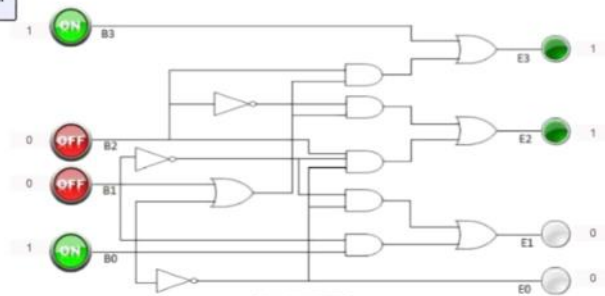

E3: 1

E2: 1

E1: 0

E0: 0

1001

Decimal : 9


BCD to Excess 3 Converter

→


1100

Decimal : 12

BCD Input

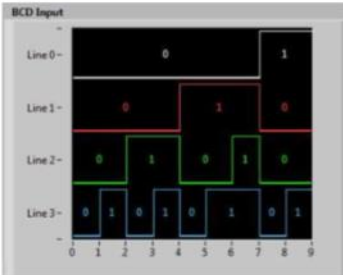

Excess 3 Input

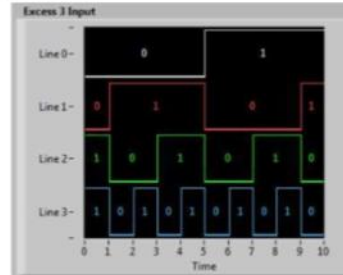


[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright ©2011 COEP Virtual Lab.

<https://be-cvnlabs.coep.in/Experiment2/index1.html>

1/1

➤ **Verification for Excess-3 to BCD Code Converter:**




Virtual Labs
 An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

Excess-3 to BCD

Run
Clear


0 OFF E3

1 ON E2

0 OFF E1

0 OFF E0

T

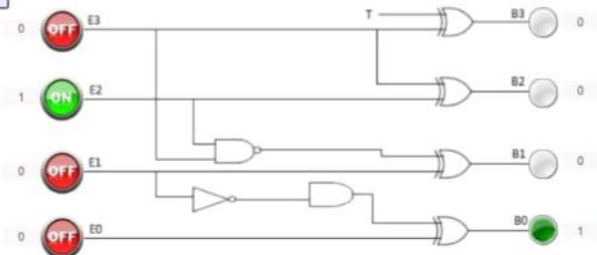

B3 0

B2 0

B1 0

B0 1

Truth Table

Excess-3				BCD			
E3	E2	E1	E0	B3	B2	B1	B0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1


0100

Excess 3 to BCD Converter


0001

Decimal : 4 Decimal : 1

Excess 3 Input

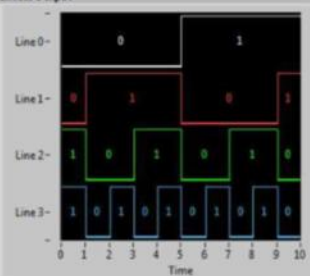

BCD Output

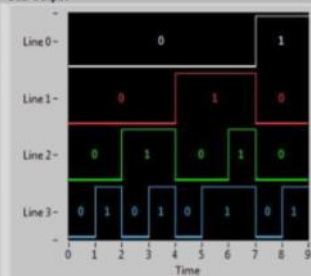


[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright ©2011 COEP Virtual Lab

<https://hv-cvnlabs.ac.in/Experiment2/index1.html>

1/1


2101227_VISHALKUMARPAJAPATI_EXPNO5 Page 18


Virtual Labs
 An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD


Run
Clear

Excess-3 to BCD

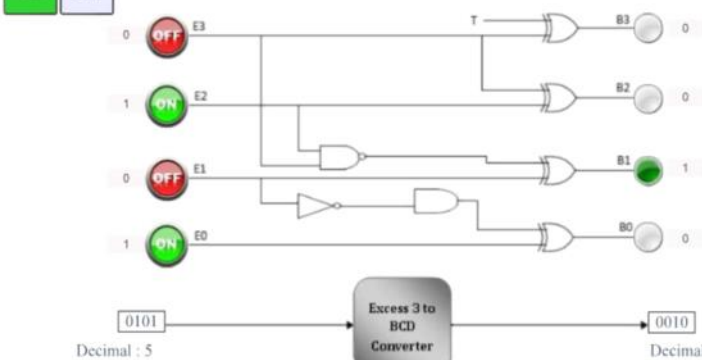


Truth Table							
Excess-3				BCD			
E3	E2	E1	E0	B3	B2	B1	B0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1

Excess 3 Input

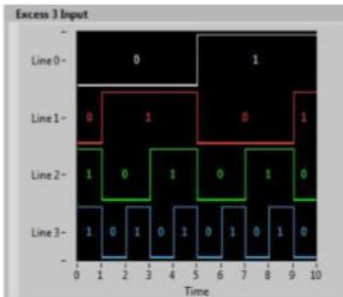


BCD Output

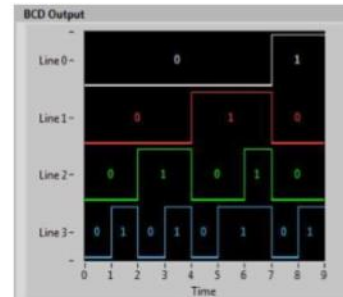

[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright ©2011 COEP Virtual Lab

https://be-cen.vlabs.ac.in/Experiment2/index1.html

1/1



An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

Excess-3 to BCD
Run Clear

0 OFF E3

1 ON E2

1 ON E1

0 OFF E0

0 B3

0 B2

1 B1

1 B0

0110

Excess 3 to BCD Converter

0011

Decimal : 6 Decimal : 3


Excess 3 Input

BCD Output

[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright © 2011 CORP Virtual Lab

<https://be-enen.vlabs.ac.in/Experiment2/index1.html>

1/1


Virtual Labs
 An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

Excess-3 to BCD

Run
Clear


0 OFF E3

1 ON E2

1 ON E1

1 ON E0

T

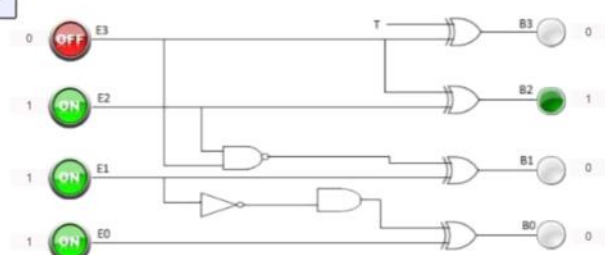

B3 0

B2 1

B1 0

B0 0

0111

Decimal : 7


0100

Decimal : 4


Truth Table

Excess-3				BCD			
E3	E2	E1	E0	B3	B2	B1	B0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1

Excess 3 Input

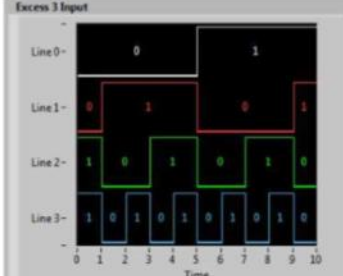

BCD Output

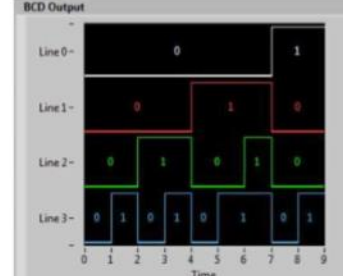


[About Us](#) | [Contact Us](#) | [Feedback](#)

Copyright ©2011 COEP Virtual Lab.

<https://he-coep-vlabs.ac.in/Experiment2/index1.html>

1/1

2101227_VISHALKUMARPAJAPATI_EXPNO5 Page 21



An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

Excess-3 to BCD

Run
Clear


1 ON E3

0 OFF E2

0 OFF E1

0 OFF E0

T

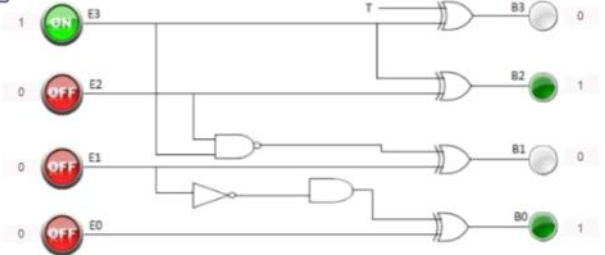

B3 0

B2 1

B1 0

B0 1

Truth Table

Excess-3				BCD			
E3	E2	E1	E0	B3	B2	B1	B0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1


1000

Excess 3 to BCD Converter


0101

Decimal : 8 Decimal : 5

Excess 3 Input

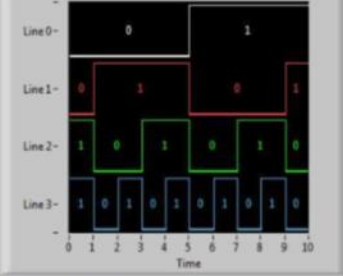

BCD Output

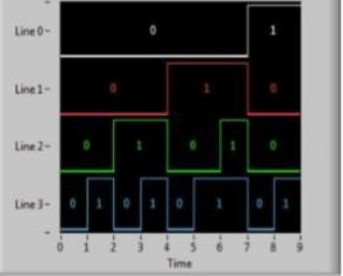


[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright ©2011 COEP Virtual Lab.

<https://he-cnen-vlabs.ac.in/Experiment2/index1.html>

1/1

2101227_VISHALKUMARPAJAPATI_EXPNO5 Page 22



An MHRD Govt of India Initiative


Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

Run
Clear

Excess-3 Inputs:

- E3: ON (1)
- E2: OFF (0)
- E1: OFF (0)
- E0: ON (1)

Logic Diagram:

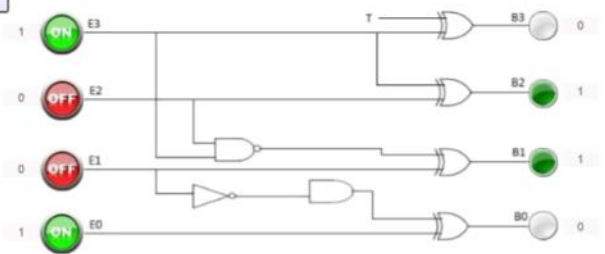


1001 (Decimal: 9) → Excess 3 to BCD Converter → 0110 (Decimal: 6)


Truth Table

Excess-3				BCD			
E3	E2	E1	E0	B3	B2	B1	B0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1

Excess 3 Input

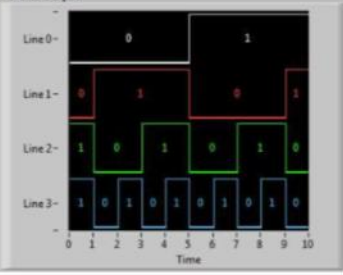


BCD Output

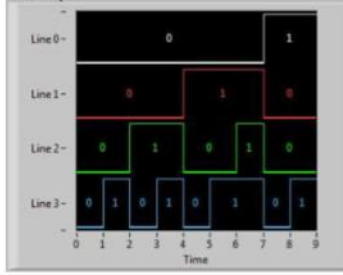

[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright ©2011 COEP Virtual Lab

<https://he-cen-vlabs.in/Experiment2/index1.html>


1/1


Virtual Labs
 An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

Excess-3 to BCD

Run
Clear

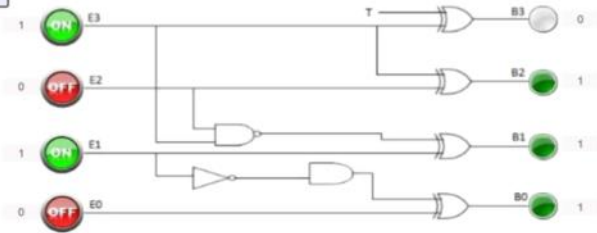

1010

Decimal : 10

Excess 3 to BCD Converter


→

0111


Decimal : 7

Excess-3				BCD			
E3	E2	E1	E0	B3	B2	B1	B0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1

Excess 3 Input

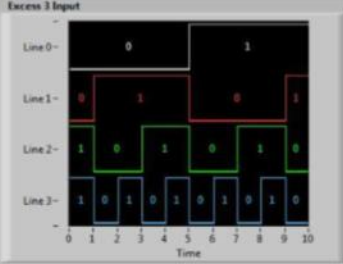


BCD Output

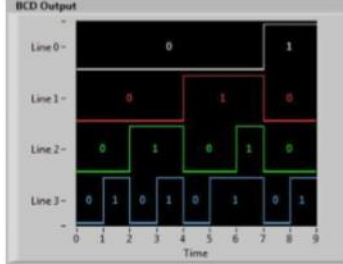

[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright ©2011 COEP Virtual Lab

https://bae-nan-vlabs.in/Experiment2/index1.html

1/1


Virtual Labs
 An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

Excess-3 to BCD

Run
Clear


1 ON E3

0 OFF E2

1 ON E1

1 ON E0

T

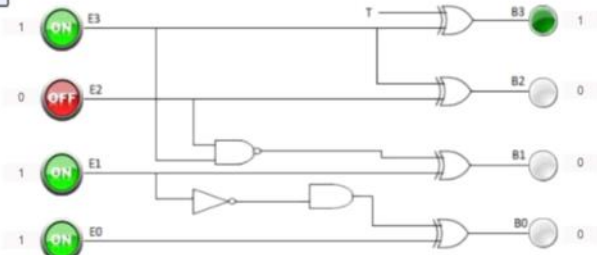

B3 1

B2 0

B1 0

B0 0

Truth Table

Excess-3				BCD			
E3	E2	E1	E0	B3	B2	B1	B0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1


1011

Excess 3 to BCD Converter


1000

Decimal : 11 Decimal : 8

Excess 3 Input

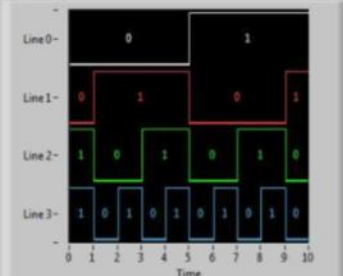

BCD Output

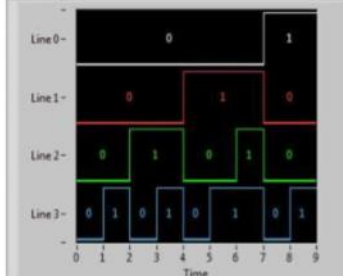


[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright ©2011 COEP Virtual Lab

https://he-mn-vlabs.an.in/Eyneriment2/index1.html

1/1

2101227_VISHALKUMARPRAJAPATI_EXPNO5 Page 25


Virtual Labs
 An MHRD Govt of India Initiative

Binary to Gray
Gray to Binary
BCD to Excess
Excess-3 to BCD

Excess-3 to BCD

Run
Clear


1 ON E3

1 ON E2

0 OFF E1

0 OFF E0

T

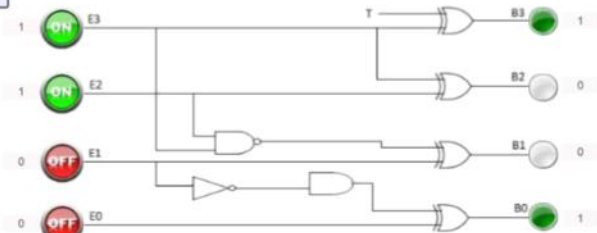

B3 1

B2 0

B1 0

B0 1


1100

Excess 3 to BCD Converter


1001

Decimal : 12 Decimal : 9

Excess 3 Input

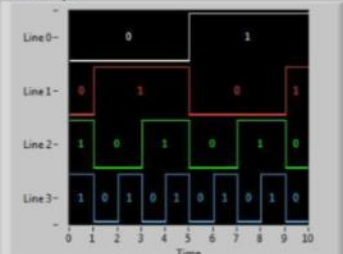

BCD Output

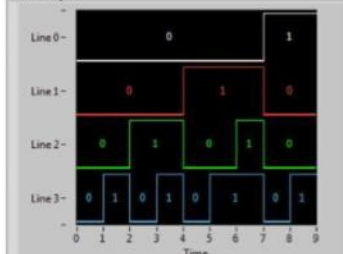

[About Us](#) | [Contact Us](#) | [Feedback](#)
 Copyright ©2011 COEP Virtual Lab

<https://he-cen-vlabs.ac.in/Experiment2/index1.html>

1/1

- **RESULT AND CONCLUSION:**

- Verified the Truth Table of Conversion of BCD to Excess 3 code.
- Verified the Truth Table of Conversion of Excess 3 to BCD code.

- **PRECAUTIONS:**

- All the connections should be made properly as per the circuit diagram.
- Connections should be tight and easy to inspect.
- Power supply should be 5v.
- Keep the switch turned off while making connections.