

EXPERIMENT NO. 10

TITLE: DESIGN AND VERIFY THE 4-BIT SERIAL IN PARALLEL OUT SHIFT REGISTERS.

▪ **OBJECTIVE:**

To analyses the circuit and truth table of 4-bit SIPO (serial input parallel output) shift register by IC 7474 (D flip flop).

▪ **APPARATUS REQUIRED:**

- Switches
- Power supply
- Resistances
- LEDs
- IC 7474(D flip flop) etc.

▪ **THEORY:**

In Serial In Parallel Out (SIPO) shift registers, the data is stored into the register serially while it is retrieved from it

in parallel-fashion. Figure 1 shows an n -bit synchronous SIPO shift register sensitive to positive edge of the clock pulse. Here the data word which is to be stored (Data in) is fed serially at the input of the first flip-flop (D_1 of FF_1). It is also seen that the inputs of all other flip-flops (except the first flip-flop FF_1) are driven by the outputs of the preceding ones like the input of FF_2 is driven by the output of FF_1 . In this kind of shift register, the data stored within the register is obtained as a parallel-output data word (Data out) at the individual output pins of the flip-flops (Q_1 to Q_n).

Table I Data Movement in Right-Shift SIPO Shift Register

Clock Cycle	Data in	Q_1	Q_2	...	Q_n
1	$B_1 \rightarrow$	B_1	0	...	0
2	$B_2 \rightarrow$	B_2	B_1	...	0
3	$B_3 \rightarrow$	B_3	B_2	...	0
4	$B_4 \rightarrow$	B_4	B_3	...	0
5	$B_5 \rightarrow$	B_5	B_4	...	0
6	$B_6 \rightarrow$	B_6	B_5	...	0
.
.
n	$B_n \rightarrow$	B_n	B_{n-1}	...	B_1

Output of SIPO (right-shift) Shift Register

Data out

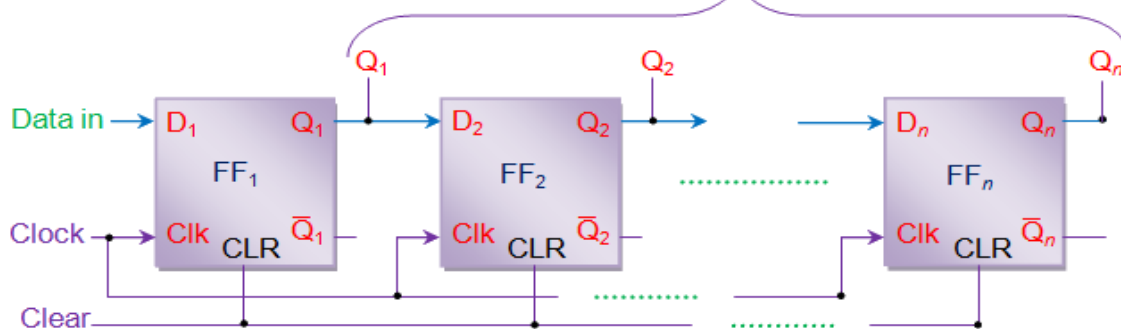


Figure 1 n -bit Serial-In Parallel-Out Right-Shift Shift Register

 


Figure 2 Output Waveform of n -bit Right-Shift SIPO Shift Register

In the right-shift SIPO shift-register, data bits shift from left to right for each clock pulse. However if the data bits are made to shift from right to left in the same design, one gets a left-shift SIPO shift-register as shown by figure 3. Nevertheless the basic working principle remains the same except the fact that now B_n down to B_1 is stored in Q_n down to Q_1 i.e. $Q_1 = B_1$, $Q_2 = B_2$... $Q_n = B_n$ at the n th clock pulse


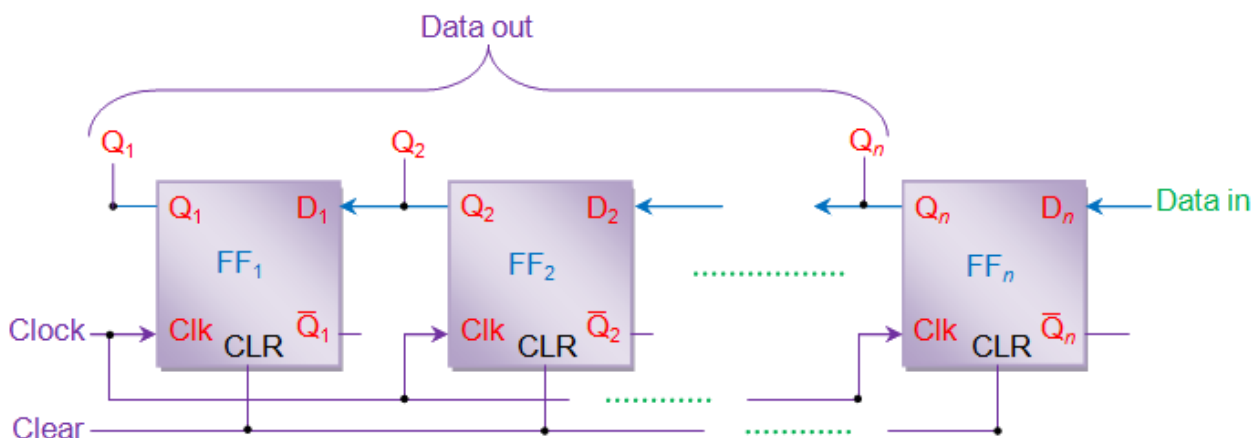


Figure 3 n -bit Serial-In Parallel-Out Left-Shift Shift Register

■ CIRCUIT DIAGRAM:

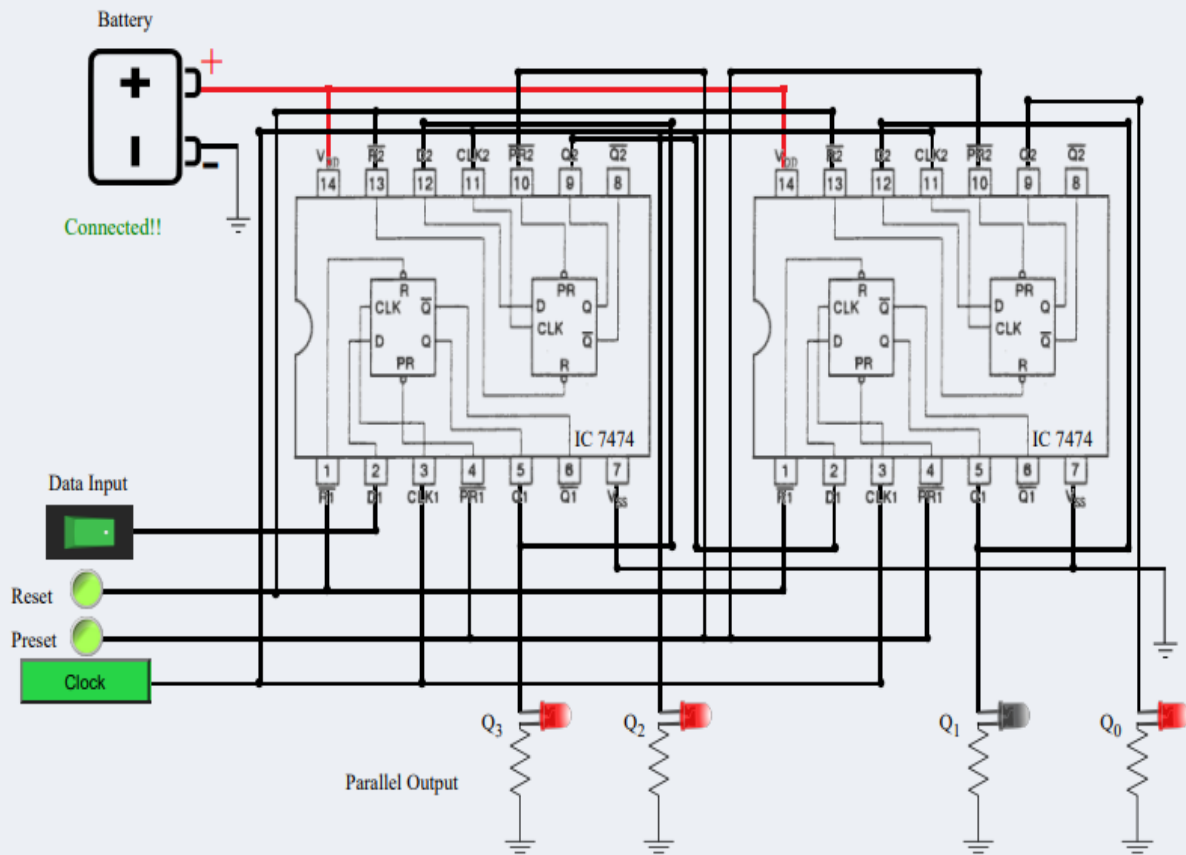Design and verification of 4-Bit Serial In Parallel Out Shift Register



TRUTH TABLE

Serial No.	Clock	Data Input	Q ₃	Q ₂	Q ₁	Q ₀
1	1	1	1	0	0	0
2	2	0	0	1	0	0
3	3	1	1	0	1	0
4	4	1	1	1	0	1

▪ **CALCULATIONS:**

▪ **TRUTH TABLE**

Serial No.	Clock	Data Input	Q ₃	Q ₂	Q ₁	Q ₀
1	1	1	1	0	0	0
2	2	0	0	1	0	0
3	3	1	1	0	1	0
4	4	1	1	1	0	1

▪ **RESULTS:**

- Verified the truth table of 4-bit SIPO (serial input parallel output) shift register by IC 7474 (D flip flop).

▪ **PRECAUTIONS:**

- All the connections should be made properly as per the circuit diagram.
- Connections should be tight and easy to inspect.
- Power supply should be 5v.
- Keep the switch turned off while making connections.