A dark blue vertical bar on the left side of the page. A blue arrow points to the right from the bar, containing the date.

2/6/2022

# EXPERIMENT NO.7

EC111

Several thin, curved lines in dark blue and light grey originate from the bottom left and curve upwards and to the right.

VISHAL KUMAR PRAJAPATI

ROLL NO. 2101227

GROUP NO.18

Name: Vishal Kumar Prayapati  
Roll. No. 2101227  
Work Bench-18


### Experiment No. 7

Aim: Implementation of Adder and Subtractor circuit.

Apparatus: breadboard, Resistors, Wires, etc.  
IC 741

Circuit Diagram:

For Inverting adder circuit:

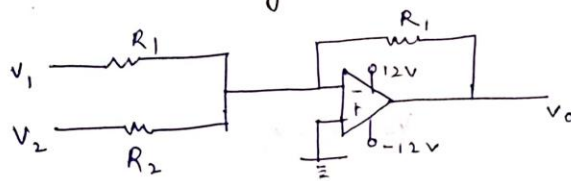

$$R_1 = R_2 = R = 1k\Omega$$


Observation:

S. No.	$V_1$	$V_2$	$V_0 = -(V_1 + V_2)$
1	2.0985	5.033	-7.041
2	4.095	5.056	-8.874
3	1.623	4.614	-6.124
4	2.578	5.584	-8.075

90  
2.6.22

for Subtractor:

Circuit diagram:

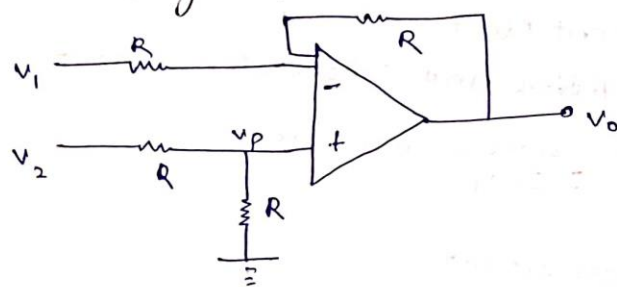

$R = 1\text{K}\Omega$

Observation:

S.No.	$V_1$	$V_2$	$V_0 = V_2 - V_1$
1	2.639	5.585	2.9734
2	1.668	5.067	3.429
3	1.0973	5.067	3.906
4	2.0619	4.547	2.522

2.6.22

# EXPERIMENT NO. 7

## TITLE: IMPLEMENTATION OF ADDER AND SUBTRACTOR CIRCUIT.

### OBJECTIVE:

- To design an adder amplifier circuit and draw the VTC.
- To design a subtractor/difference amplifier circuit and draw the VTC

### APPARATUS REQUIRED:

- Breadboard
- Connecting wires
- Resister
- Power supply
- 741 IC (op-amp)

### THOREY:

#### **ADDER:**

An adder is an electronic circuit that produces an output, which is equal to the sum of the applied inputs. This section discusses

the op-amp-based adder circuit. An op-amp-based adder produces an output equal to the sum of the input voltages applied at its inverting terminal. It is also called a summing amplifier since the output is an amplified one.

### **FORMULA USED:**

$$V_o = - ( ( R_f / R_1 ) V_1 + ( R_f / R_2 ) V_2 + ( R_f / R_3 ) V_3 )$$

If  $R_f = R_1 = R_2 = R_3 = R$  in ohms

Therefore,  $V_o = -( V_1 + V_2 + V_3 )$

### **SUBTRACTOR:**

A subtractor is an electronic circuit that produces an output, which is equal to the difference between the applied inputs. This section discusses the op-amp-based subtractor circuit. An op-amp-based subtractor produces an output equal to the difference between the input voltages applied at its inverting and non-inverting terminals. It is also called a difference amplifier since the output is an amplified one.


### **FORMULA USED:**

$$V_o = ( R_2 / R_1 ) * ( V_2 - V_1 )$$


If  $R_2 = R_1 = R$  then,  $V_o = ( V_2 - V_1 )$

### **CIRCUIT DIAGRAM:**

### **ADDER:**

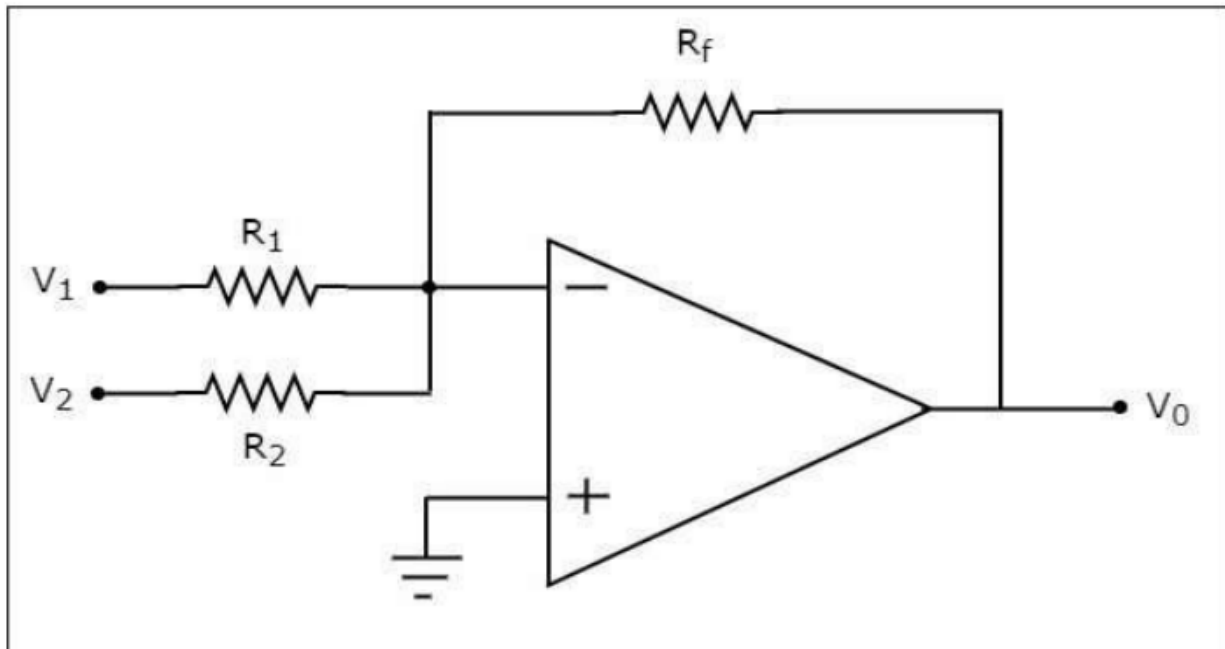

**SUBTRACTOR:**

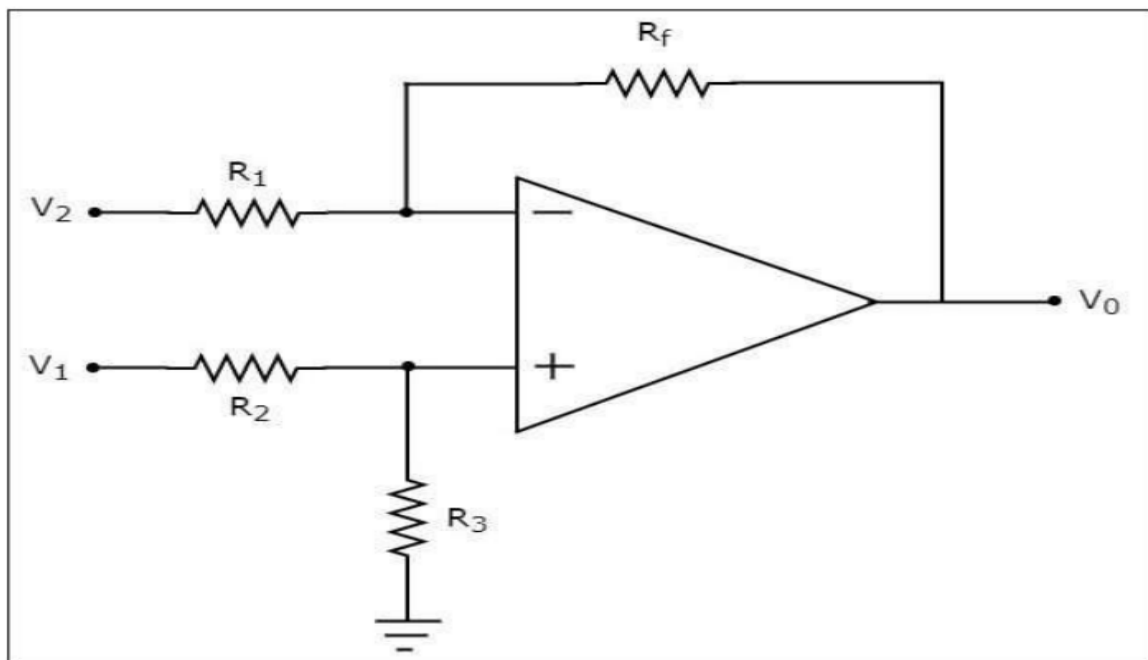

**OBSERVATION:**

## **ADDER:**

S.NO.	V1	V2	$V_0=-(V_1+V_2)$
1	2.095	5.033	-7.041
2	4.095	5.056	-8.874
3	1.623	4.614	-6.124
4	2.578	5.584	-8.075

## **SUBTRACTOR:**

S.NO.	V1	V2	$V_0=(V_2-V_1)$
1	2.639	5.585	2.9734
2	1.668	5.067	3.429
3	1.0973	5.067	3.906
4	2.0619	4.547	2.522

## **RESULT:**

- Successfully verified the adder amplifier circuit.
- Successfully verified the subtractor amplifier circuit.

## **PRECAUTIONS:**

- Connections should be made accordingly to the circuit diagram only.
- Do not be on the DC power supply for a long time otherwise diode may be burned.
- Wires should be tight and no short-circuiting should be there.
- Do not cross the maximum power rating.